

## **Lab 4B(Lab 4 Part-2): Data-Path Design:**

### **Introduction:**

The objective of this lab(lab 4 part 2) is to successfully construct a functional data-path scheme and test it for a processor, more specifically a 32-bit CPU unit. For this lab, previous lab components(PC, register, ALU, Data memory module) are taken side-by-side with some new data-path components, and they are assembled to create a sufficient CPU data-path. The data-path is then required to go through testing from different specifications and requirements in creating different waveforms for various operations. Note that the instruction memory is not filled out yet, this will be worked on for later labs(lab 6).

Please note that the following project files are the components from the previous labs that are required for this one:

**i** In this lab we will build the and test the data-path for the 32-bit processor. Please copy the following VHDL files from the previous labs into your Lab4b folder, then add them to your project in the Add Files section of the New Project Wizard:

- From Lab 2:
  - "register32.vhd"
  - "add.vhd"
  - "mux2to1.vhd"
  - "pc.vhd"
- From Lab 3a:
  - "fulladd.vhd"
  - "adder4.vhd"
  - "adder16.vhd"
  - "adder32.vhd"
  - "alu.vhd"
- From Lab 4a:
  - "data\_mem.vhd"

The following are the new components that are required for the data-path:

Implementation of the LZE(Lower Zero Extender) Unit:

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity LZE is
6  port(
7    LZE_in : in std_logic_vector(31 downto 0);
8    LZE_out : out std_logic_vector(31 downto 0)
9  );
10 end entity;
11
12 architecture Behavior of LZE is
13   signal zeros: std_logic_vector(15 downto 0) := (others => '0');
14 begin
15   LZE_out <= zeros & LZE_in(15 downto 0);
16 end Behavior;

```

Figure 1: Code Implementation for the LZE(Lower Zero Extender) Unit Component

Implementation of the UZE(Upper Zero Extender) Unit:

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity UZE is
6  port(
7    UZE_in : in std_logic_vector(31 downto 0);
8    UZE_out : out std_logic_vector(31 downto 0)
9  );
10 end entity;
11
12 architecture Behavior of UZE is
13   signal zeros : std_logic_vector(15 downto 0) := (others => '0');
14 begin
15   UZE_out <= UZE_in(15 downto 0) & zeros;
16 end Behavior;

```

Figure 2: Code Implementation for the UZE(Upper Zero Extender) Unit Component

Implementation of the RED(Reducer Unit) Unit:

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity RED is
6  port(
7      RED_in    : in  std_logic_vector(31 downto 0);
8      RED_out    : out unsigned(7 downto 0)
9  );
10 end entity;
11
12 architecture Behavior of RED is
13 begin
14     RED_out <= unsigned (RED_in(7 downto 0));
15 end Behavior;
16
```

Figure 3: Code Implementation for the RED(Reducer Unit) Unit Component

Implementation of the mux4to1(4 IN-1 OUT MUX) Unit:

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity mux4to1 is
5  port(
6      s : in std_logic_vector(1 downto 0);
7      X1, X2, X3, X4 : in std_logic_vector(31 downto 0);
8      f: out std_logic_vector(31 downto 0)
9  );
10 end mux4to1;
11
12 architecture Behavior of mux4to1 is
13 begin
14     with s select
15         f <= X1 when "00",
16             X2 when "01",
17             X3 when "10",
18             X4 when "11";
19 end Behavior;

```

Figure 4: Code Implementation for the 4 Input and 1 Output MUX(mux4to1) Unit Component

## Implementation of the 32-bit CPU Data Path Design:

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  use ieee.std_logic_unsigned.all;
5
6  entity data_path is
7  port(
8      --Clock Signals
9      Clk, mClk : in std_logic;
10
11      --Memory Signals
12      WEN, EN : in std_logic;
13
14      --Register Control Signals
15      Clr_A, Ld_A : in std_logic;
16      Clr_B, Ld_B : in std_logic;
17      Clr_C, Ld_C : in std_logic;
18      Clr_Z, Ld_Z : in std_logic;
19      Clr_PC, Ld_PC : in std_logic;
20      Clr_IR, Ld_IR : in std_logic;
21
22      --Register Outputs
23      Out_A : out std_logic_vector(31 downto 0);
24      Out_B : out std_logic_vector(31 downto 0);
25      Out_C : out std_logic;
26      Out_Z : out std_logic;
27      Out_PC : out std_logic_vector(31 downto 0);
28      Out_IR : out std_logic_vector(31 downto 0);
29
30      --Special PC Inputs
31      Inc_PC : in std_logic;
32
33      --Address and Data Bus Signals
34      ADDR_OUT : out std_logic_vector(31 downto 0);
35      DATA_IN : in std_logic_vector(31 downto 0);
36      DATA_BUS, MEM_OUT, MEM_IN : out std_logic_vector(31 downto 0);
37      MEM_ADDR : out unsigned(7 downto 0);
38
39      --MUX Controls
40      DATA_MUX : in std_logic_vector(1 downto 0);
41      REG_MUX : in std_logic;
42      A_MUX, B_MUX : in std_logic;
43      IM_MUX1 : in std_logic;
44      IM_MUX2 : in std_logic_vector(1 downto 0);
45
46      --ALU Operations
47      ALU_Op : in std_logic_vector(2 downto 0)
48  );
49  end entity;
50
51
52  architecture Behavior of data_path is
53  --Component Instantiations Data Memory Module
54  component data_mem is
55  port(
56      clk : in std_logic;
57      addr : in unsigned(7 downto 0);
58      data_in : in std_logic_vector(31 downto 0);
59      wen : in std_logic;
60      en : in std_logic;
61      data_out : out std_logic_vector(31 downto 0)
62  );
63  end component;
64
65
```

```

66 | --Register32
67 | component register32 is
68 | port (
69 |   d : in std_logic_vector(31 downto 0) ;
70 |   ld : in std_logic ;
71 |   clr : in std_logic ;
72 |   clk : in std_logic ;
73 |   Q : out std_logic_vector(31 downto 0)) ;
74 | end component;
75 |
76 | --Program Counter
77 | component pc is
78 | port (
79 |   clr : in std_logic ;
80 |   clk : in std_logic ;
81 |   ld : in std_logic ;
82 |   inc : in std_logic ;
83 |   d : in std_logic_vector(31 downto 0) ;
84 |   q : out std_logic_vector(31 downto 0) ) ;
85 | end component;
86 |
87 | --LZE
88 | component LZE is
89 | port(
90 |   LZE_in : in std_logic_vector(31 downto 0);
91 |   LZE_out : out std_logic_vector(31 downto 0)
92 | );
93 | end component;
94 |
95 | --UZE
96 | component UZE is
97 | port(
98 |   UZE_in : in std_logic_vector(31 downto 0);
99 |   UZE_out : out std_logic_vector(31 downto 0)
100 | );
101 | end component;
102 |
103 | --RED
104 | component RED is
105 | port(
106 |   RED_in : in std_logic_vector(31 downto 0);
107 |   RED_out : out unsigned(7 downto 0)
108 | );
109 | end component;
110 |
111 | --mux2to1
112 | component mux2to1 is
113 | port (
114 |   s : in std_logic ;
115 |   w0, w1 : in std_logic_vector(31 downto 0) ;
116 |   f : out std_logic_vector(31 downto 0) ) ;
117 | end component;
118 |
119 | --mux4to1
120 | component mux4to1 is
121 | port(
122 |   s : in std_logic_vector(1 downto 0);
123 |   X1, X2, X3, X4 : in std_logic_vector(31 downto 0);
124 |   f: out std_logic_vector(31 downto 0)
125 | );
126 | end component;
127 |
128 | --ALU
129 | component ALU32 is
130 | port(
131 |   a, b : in std_logic_vector(31 downto 0);
132 |   op : in std_logic_vector(2 downto 0);
133 |   result : out std_logic_vector(31 downto 0);
134 |   zero, cout : out std_logic );
135 | end component;
136 |

```

```

137 --Signal Instantiations
138 signal IR_OUT : std_logic_vector(31 downto 0);
139 signal data_bus_s : std_logic_vector(31 downto 0);
140 signal LZE_out_PC : std_logic_vector(31 downto 0);
141 signal LZE_out_A_mux : std_logic_vector(31 downto 0);
142 signal LZE_out_B_mux : std_logic_vector(31 downto 0);
143 signal RED_out_data_mem : unsigned(7 downto 0);
144 signal A_Mux_out : std_logic_vector(31 downto 0);
145 signal B_Mux_out : std_logic_vector(31 downto 0);
146 signal reg_A_out : std_logic_vector(31 downto 0);
147 signal reg_B_out : std_logic_vector(31 downto 0);
148 signal reg_Mux_out : std_logic_vector(31 downto 0);
149 signal data_mem_out : std_logic_vector(31 downto 0);
150 signal UZE_IM_MUX1_out : std_logic_vector(31 downto 0);
151 signal IM_MUX1_out : std_logic_vector(31 downto 0);
152 signal LZE_IM_MUX2_out : std_logic_vector(31 downto 0);
153 signal IM_MUX2_out : std_logic_vector(31 downto 0);
154 signal ALU_out : std_logic_vector(31 downto 0);
155 signal zero_flag : std_logic;
156 signal carry_flag : std_logic;
157 signal temp : std_logic_vector(30 downto 0) := (others => '0');
158 signal out_pc_sig : std_logic_vector(31 downto 0);
159
160 begin
161   IR: register32 port map(
162     data_bus_s,
163     Ld_IR,
164     ClrIR,
165     Clk,
166     IR_OUT
167   );
168
169   LZE_PC: LZE port map(
170     IR_OUT,
171     LZE_out_PC
172   );
173
174   PC0: pc port map(
175     CLRPC,
176     Clk,
177     Ld_PC,
178     INC_PC,
179     LZE_out_PC,
180     --ADDR_OUT
181     out_pc_sig
182   );
183
184   LZE_A_Mux: LZE port map(
185     IR_OUT,
186     LZE_out_A_mux
187   );
188
189   A_Mux0: mux2to1 port map(
190     A_MUX,
191     data_bus_s,
192     LZE_out_A_mux,
193     A_mux_out
194   );
195
196   Reg_A: register32 port map(
197     A_mux_out,
198     Ld_A,
199     Clr_A,
200     Clk,
201     reg_A_out
202   );
203
204   LZE_B_Mux: LZE port map(
205     IR_OUT,
206     LZE_out_B_mux
207   );
208

```

```

209  B_Mux0: mux2to1 port map(
210  | B_MUX,
211  | data_bus_s,
212  | LZE_out_B_mux,
213  | B_mux_out
214  | );
215  |
216  Reg_B: register32 port map(
217  | B_mux_out,
218  | Ld_B,
219  | Clr_B,
220  | Clk,
221  | reg_B_out
222  | );
223  |
224  Reg_Mux0: mux2to1 port map(
225  | REG_MUX,
226  | Reg_A_out,
227  | Reg_B_out,
228  | Reg_Mux_out
229  | );
230  |
231  RED_Data_Mem: RED port map(
232  | IR_OUT,
233  | RED_out_data_mem
234  | );
235  |
236  Data_Mem0: data_mem port map(
237  | mClk,
238  | RED_out_data_mem,
239  | Reg_Mux_out,
240  | WEN,
241  | EN,
242  | data_mem_out
243  | );
244  |
245  UZE_IM_MUX1: UZE port map(
246  | IR_OUT,
247  | UZE_IM_MUX1_out
248  | );
249  |
250  IM_MUX1a: mux2to1 port map(
251  | IM_MUX1,
252  | reg_A_out,
253  | UZE_IM_MUX1_out,
254  | IM_MUX1_out
255  | );
256  |
257  LZE_IM_MUX2: LZE port map(
258  | IR_OUT,
259  | LZE_IM_MUX2_out
260  | );
261  |
262  IM_MUX2a: mux4to1 port map(
263  | IM_MUX2,
264  | reg_B_out,
265  | LZE_IM_MUX2_out, (temp &'1'), (others =>'0'),
266  | IM_MUX2_out
267  | );
268  |
269  ALU0: ALU32 port map(
270  | IM_MUX1_out,
271  | IM_MUX2_out,
272  | ALU_Op,
273  | ALU_out,
274  | zero_flag,
275  | carry_flag
276  | );
277  |

```

```

278 DATA_MUX0: mux4to1 port map(
279     DATA_MUX,
280     DATA_IN,
281     data_mem_out,
282     ALU_out,
283     (others => '0'),
284     data_bus_s
285 );
286
287 DATA_BUS <= data_bus_s;
288 OUT_A <= reg_A_out;
289 OUT_B <= reg_B_out;
290 OUT_IR <= IR_OUT;
291 ADDR_OUT <= out_pc_sig;
292 OUT_PC <= out_pc_sig;
293
294 MEM_ADDR <= RED_out_data_mem;
295 MEM_IN <= Reg_Mux_out;
296 MEM_OUT <= data_mem_out;
297
298 end Behavior;

```

Figure 5 – 1: Code Implementation for the 32-bit CPU Data Path Design Component

### Data Path Functional Simulation Waveforms - Testing Portion:

1)

 


Figure 6: Waveform of the 32-bit CPU Data Path Design Component for operation: LDAI(load)



2)

 


Figure 7: Waveform of the 32-bit CPU Data Path Design Component for operation: LDBI(load)

3)

 


Figure 8: Waveform of the 32-bit CPU Data Path Design Component for operation: STA(storing)

4)

 


Figure 9: Waveform of the 32-bit CPU Data Path Design Component for operation: STB(storing)

5)

 


Figure 10: Waveform of the 32-bit CPU Data Path Design Component for operation: LDA(load)

6)

 


Figure 11: Waveform of the 32-bit CPU Data Path Design Component for operation: LDB(load)

7)

 


Figure 12 Waveform of the 32-bit CPU Data Path Design for operation: LUI(load-instr)

8)

 


Figure 13: Waveform of the 32-bit CPU Data Path Design Component for operation: JMP

9)

 


Figure 14: Waveform of the 32-bit CPU Data Path Design Component for operation: ANDI (and-intermediate)

10)

 


Figure 15: Waveform of the CPU Data Path Design for operation: ADDI(Add-intermediate)

11)

 


Figure 16: Waveform of the 32-bit CPU Data Path Design for operation: ORI(Or-intermediate)

12)

 


Figure 17: Waveform of the 32-bit CPU Data Path Design for operation: ADD

13)

 


Figure 18: Waveform of the 32-bit CPU Data Path Design for operation: SUB

14)

 


Figure 19: Waveform of the 32-bit CPU Data Path Design for operation: DECA(Decrement)

15)

 


Figure 20: Waveform of the 32-bit CPU Data Path Design for operation: INCA(Increment)

16)

 


Figure 21: Waveform of the 32-bit CPU Data Path Design for operation: ROL(Rotate Left)

17)

 


Figure 22: Waveform of the 32-bit CPU Data Path Design for operation: ROR(Rotate Right)



18)

 


Figure 23: Waveform of the 32-bit CPU Data Path Design for operation: CLRA (Clear A reg)

19)

 


Figure 24: Waveform of the 32-bit CPU Data Path Design for operation: CLRB(Clear B reg)

## Final END Questions:

```
300 --END Questions:
301 --1) a)INCA: The Increment Function is implemented by placing Reg A as the first ALU input, by loading and opening the MUX(IM_MUX1) And the other input for the ALU
302 -- is a single value '1'(by setting IM_MUX2 to 2). Reg A and '1' are added in the ALU(OpCode = 010)
303 -- b)ADDI: The Adding with intermediate function is implemented by enabling the mux and loading reg A as one of the input. The other input would be the DATA_IN
304 -- that is directly loaded to the IR reg, from there it makes it's way to the second input(where IM_MUX2 is set as 1). Reg A and the DATA_IN value in
305 -- Reg IR are then added (OpCode = 010)
306 -- c)LDBI: The Loading B with intermediate function is implemented by first loading IR reg with the DATA_IN value. Then the B_mux and load for Reg B is enabled
307 -- allowing the DATA_IN from IR Reg to make its way there, and thus the DATA_IN value is loaded into reg B .
308 -- d)LDA: The Load memory with A function takes the first DATA_IN input and enables the A_MUX and loades reg A with it. Now this function uses the Data Memory
309 -- unit; the reg A is used as the data_in for memory, and the next DATA_IN from the cpu is the specified address to where the contents of reg A will be
310 -- stored. The address(last 2 of the 8 hex) comes form the IR reg and the data memory unit is in writing mode(WEN=1 and EN=1), where the contents of reg A
311 -- will be written in the address. Later reg A is cleared and data_in is no longer in use. Now the same address is accessed by loading it in the IR reg
312 -- again, but this time it is in read mode(just EN=1), and the memory unit generates output(content of regA that was written previously).
313
314 --2) The Maximum Reliable clock speed is determined by the delays that indicate the time required to execute the process. Most specifically the longest
315 -- combinational delay from the time it takes to progress through the combinational logic gate circuit, that is the "Critical Path Delay".
316 -- The clock period, T_clk must be atleast as long as T_criticalpathdelay: Tclk >= T_criticalpathdelay
317 -- The Reliable clock speed also includes the setup time, since data signals must be settled before the clock edge, and data must remain stable after the clock
318 -- cycle ends(T_setup):
319 -- Thus, the acceptable Maximum Reliable clock speed must include two factors, the critical path delay and setup time:
320 -- T_clk = T_criticalpathdelay + T_setup
321
322 --3) The reliable limit for the data-path clock is(in frequency):
323 -- f_reliable_clk = 1 / (T_criticalpathdelay + T_setup)
324 -- f_reliable_clk = 1 / (20 ns + 1 ns) [The critica path delay is assumed to be the current clock cycle that is successful(20ns); the setup time is assumed to
325 -- be lns as per usual cirumstances]
326 -- f_reliable_clk = 1 / (20 ns + 1 ns) = 1 / (21 ns) = 47.6 MHz
327
```

Figure 5 – 2: END Questions for Data Path Design Component